

**2024**

( NEP-2020 )

( 2nd Semester )

**PHYSICS (MAJOR/MINOR)**

**( Basic Electronics )**

Full Marks : 75

Time : 3 hours

*The figures in the margin indicate full marks for the questions*

**( SECTION : A—OBJECTIVE )**

( Marks : 10 )

Tick (✓) the correct answer in the brackets provided :

1×10=10

1. The leakage current across a *p-n* junction is due to

- (a) impurity ( )
- (b) minority carriers ( )
- (c) majority carriers ( )
- (d) junction capacitance ( )

2. The ripple factor of a full-wave rectifier is

(a) 1.21 ( )

(b) 1.11 ( )

(c) 0.48 ( )

(d) 0.81 ( )

3. A  $p$ - $n$  junction that radiates energy as light is called a/an

(a) photodiode ( )

(b) LED ( )

(c) Zener diode ( )

(d) Schottky diode ( )

4. Doping concentration of a  $p$ - $n$ - $p$  transistor is lowest in the

(a)  $p$ -region ( )

(b)  $n$ -region ( )

(c) collector ( )

(d) emitter ( )

5. In a CB configuration transistor output characteristics, the region above  $V_{CB} = 0$  and  $I_E = 0$  is known as

(a) saturation region ( )

(b) input region ( )

(c) active region ( )

(d) cut-off region ( )

6. In the DC loadline, the point where the loadline intersects the Y axis is

(a) cut-off point ( )

(b) critical point ( )

(c) saturation point ( )

(d) subcritical point ( )

7. The efficiency of a class-A amplifier is

(a) 25% ( )

(b) 35% ( )

(c) 40% ( )

(d) 60% ( )

8. In a negative feedback amplifier, phase shift between the input and output signals is

(a)  $0^\circ$  ( )

(b)  $90^\circ$  ( )

(c)  $180^\circ$  ( )

(d)  $360^\circ$  ( )

9. The output voltage in Hartley oscillator is the voltage drop across

(a)  $L_1$  ( )

(b)  $L_2$  ( )

(c)  $M$  ( )

(d)  $C$  ( )

10. In a CRO, time-varying signals are displayed in

(a) 1-dimension ( )

(b) 2-dimension ( )

(c) 3-dimension ( )

(d) 4-dimension ( )

**( SECTION : B—SHORT ANSWERS )**

( Marks : 15 )

Answer *five* of the following, taking at least *one* from each Unit :

3×5=15

**UNIT—I**

1. Show that the rectification efficiency of half-wave rectifier is 40.6%.
2. Discuss in brief the static and dynamic resistances.

**UNIT—II**

3. Explain DC load line of a transistor with a neat diagram.
4. Prove the relation,  $\alpha = \frac{\beta}{1 + \beta}$ , where the symbols have their usual meanings.

**UNIT—III**

5. With a suitable diagram, describe class-A amplifier.
6. Compare positive and negative feedback of an amplifier.

**UNIT—IV**

7. Write the Barkhausen's criterion for self-sustained oscillations.
8. Explain the measurement of voltage and current in a CRO.

( SECTION : C—DESCRIPTIVE )

( Marks : 50 )

Answer five of the following, taking at least one from each Unit :

10×5=50

UNIT—I

1. (a) Explain the current flow mechanism in reverse biased diode.  
(b) With graphical illustration, describe the  $I$ - $V$  characteristics of a  $p$ - $n$  junction diode.  
(c) What is voltage regulation? Explain how Zener diode is used as a voltage regulator. 1+3=4
2. (a) Describe the working of light-emitting diode.  
(b) Illustrate with diagram, the principle, construction and working of a photodiode.  
(c) Explain filter in electronics. Describe the filtering action of  $\pi$  filter. 1+3=4

UNIT—II

3. (a) What is thermal runaway in a transistor?  
(b) Discuss the construction and working of a  $p$ - $n$ - $p$  transistor with diagram.  
(c) What is CE configuration in an  $n$ - $p$ - $n$  transistor? Explain with diagram, the input and output characteristics of CE configuration in an  $n$ - $p$ - $n$  transistor. 1+4=5
4. (a) Explain voltage and current gain of a transistor.  
(b) What is a voltage divider circuit? Show how it prevents operating point changes.  
(c) Describe base width modulation and transition time of a transistor. 3  
4



### UNIT—III

5. (a) What is an R-C coupled amplifier? Explain in detail its frequency response. 4
- (b) Describe the working, power output and efficiency of the following amplifiers with suitable diagrams : 3×2=6
- (i) Class-B push-pull amplifier
  - (ii) Class-AB amplifiers
6. (a) Write notes on power dissipation and distortion of an amplifier. 4
- (b) Explain in particular the effect of negative feedback on the following : 2×3=6
- (i) Input impedance
  - (ii) Gain
  - (iii) Noise

### UNIT—IV

7. (a) What are sinusoidal and relaxation oscillators? Explain the working principle of oscillators. 3
- (b) Mention at least three advantages of phase-shift oscillator. 3
- (c) Illustrate in detail Colpitts' oscillator using appropriate circuit diagram. 4
8. (a) What is CRO? Draw and explain the block diagram of basic CRO. 3
- (b) With appropriate diagram, describe the specifications of a CRO and their significance. 3
- (c) Using a neat diagram, explain in detail the construction of CRT. What are electrostatic focusing and acceleration in an electron gun? 4

\*\*\*

2024

( NEP-2020 )

( 2nd Semester )

**PHYSICS (MAJOR/MINOR)**

**( Basic Electronics )**

Full Marks : 75

Time : 3 hours

*The figures in the margin indicate full marks for the questions*

**( SECTION : A—OBJECTIVE )**

( Marks : 10 )

Tick (✓) the correct answer in the brackets provided :

1×10=10

1. The leakage current across a  $p$ - $n$  junction is due to

- (a) impurity ( )
- (b) minority carriers ( )
- (c) majority carriers ( )
- (d) junction capacitance ( )



2. The ripple factor of a full-wave rectifier is

(a) 1.21 ( )

(b) 1.11 ( )

(c) 0.48 ( )

(d) 0.81 ( )

3. A  $p$ - $n$  junction that radiates energy as light is called a/an

(a) photodiode ( )

(b) LED ( )

(c) Zener diode ( )

(d) Schottky diode ( )

4. Doping concentration of a  $p$ - $n$ - $p$  transistor is lowest in the

(a)  $p$ -region ( )

(b)  $n$ -region ( )

(c) collector ( )

(d) emitter ( )

5. In a CB configuration transistor output characteristics, the region above  $V_{CB} = 0$  and  $I_E = 0$  is known as

(a) saturation region ( )

(b) input region ( )

(c) active region ( )

(d) cut-off region ( )

6. In the DC loadline, the point where the loadline intersects the Y axis is

(a) cut-off point ( )

(b) critical point ( )

(c) saturation point ( )

(d) subcritical point ( )

7. The efficiency of a class-A amplifier is

(a) 25% ( )

(b) 35% ( )

(c) 40% ( )

(d) 60% ( )

8. In a negative feedback amplifier, phase shift between the input and output signals is

(a)  $0^\circ$  ( )

(b)  $90^\circ$  ( )

(c)  $180^\circ$  ( )

(d)  $360^\circ$  ( )

9. The output voltage in Hartley oscillator is the voltage drop across

(a)  $L_1$  ( )

(b)  $L_2$  ( )

(c)  $M$  ( )

(d)  $C$  ( )

10. In a CRO, time-varying signals are displayed in

(a) 1-dimension ( )

(b) 2-dimension ( )

(c) 3-dimension ( )

(d) 4-dimension ( )

**( SECTION : B—SHORT ANSWERS )**

**( Marks : 15 )**

Answer *five* of the following, taking at least *one* from each Unit :

**3×5=15**

**UNIT—I**

1. Show that the rectification efficiency of half-wave rectifier is 40.6%.
2. Discuss in brief the static and dynamic resistances.

**UNIT—II**

3. Explain DC load line of a transistor with a neat diagram.
4. Prove the relation,  $\alpha = \frac{\beta}{1 + \beta}$ , where the symbols have their usual meanings.

**UNIT—III**

5. With a suitable diagram, describe class-A amplifier.
6. Compare positive and negative feedback of an amplifier.

**UNIT—IV**

7. Write the Barkhausen's criterion for self-sustained oscillations.
8. Explain the measurement of voltage and current in a CRO.

( SECTION : C—DESCRIPTIVE )

( Marks : 50 )

Answer *five* of the following, taking at least *one* from each Unit :

10×5=50

UNIT—I

1. (a) Explain the current flow mechanism in reverse biased diode. 2
- (b) With graphical illustration, describe the  $I$ - $V$  characteristics of a  $p$ - $n$  junction diode. 4
- (c) What is voltage regulation? Explain how Zener diode is used as a voltage regulator. 1+3=4
2. (a) Describe the working of light-emitting diode. 2
- (b) Illustrate with diagram, the principle, construction and working of a photodiode. 4
- (c) Explain filter in electronics. Describe the filtering action of  $\pi$  filter. 1+3=4

UNIT—II

3. (a) What is thermal runaway in a transistor? 2
- (b) Discuss the construction and working of a  $p$ - $n$ - $p$  transistor with diagram. 3
- (c) What is CE configuration in an  $n$ - $p$ - $n$  transistor? Explain with diagram, the input and output characteristics of CE configuration in an  $n$ - $p$ - $n$  transistor. 1+4=5
4. (a) Explain voltage and current gain of a transistor. 3
- (b) What is a voltage divider circuit? Show how it prevents operating point changes. 3
- (c) Describe base width modulation and transition time of a transistor. 4

### UNIT—III

5. (a) What is an R-C coupled amplifier? Explain in detail its frequency response. 4
- (b) Describe the working, power output and efficiency of the following amplifiers with suitable diagrams :  $3 \times 2 = 6$
- (i) Class-B push-pull amplifier
  - (ii) Class-AB amplifiers
6. (a) Write notes on power dissipation and distortion of an amplifier. 4
- (b) Explain in particular the effect of negative feedback on the following :  $2 \times 3 = 6$
- (i) Input impedance
  - (ii) Gain
  - (iii) Noise

### UNIT—IV

7. (a) What are sinusoidal and relaxation oscillators? Explain the working principle of oscillators. 3
- (b) Mention at least three advantages of phase-shift oscillator. 3
- (c) Illustrate in detail Colpitts' oscillator using appropriate circuit diagram. 4
8. (a) What is CRO? Draw and explain the block diagram of basic CRO. 3
- (b) With appropriate diagram, describe the specifications of a CRO and their significance. 3
- (c) Using a neat diagram, explain in detail the construction of CRT. What are electrostatic focusing and acceleration in an electron gun? 4

\*\*\*