

2025

(NEP—2020)

(2nd Semester)

PHYSICS (MAJOR/MINOR)

(Basic Electronics)

Full Marks : 75

Time : 3 hours

The figures in the margin indicate full marks for the questions

(SECTION : A—OBJECTIVE)

(Marks : 10)

Tick (✓) the correct answer in the brackets provided :

1×10=10

1. The reverse saturation current across a p - n junction is due to

- (a) minority carriers ()
- (b) majority carriers ()
- (c) depletion width ()
- (d) junction capacitance ()

2. Ripple factor of a half-wave rectifier is

(a) 1.21 ()

(b) 1.11 ()

(c) 0.48 ()

(d) 0.81 ()

3. A p - n junction that absorbs light energy to produce current is called a/an

(a) LED ()

(b) photodiode ()

(c) tunnel diode ()

(d) Zener diode ()

4. In P - N - P transistor, doping concentration is highest in the

(a) P -region ()

(b) N -region ()

(c) collector ()

(d) emitter ()

5. In a CB configuration transistor output characteristics, the region on the left side of $V_{CB} = 0$ is known as

- (a) input region ()
- (b) active region ()
- (c) cut-off region ()
- (d) saturation region ()

6. DC loadline of a transistor is a straight line drawn in graph between

- (a) I_C and V_{CB} ()
- (b) I_E and V_{CB} ()
- (c) I_C and V_{CE} ()
- (d) V_{CE} and V_{CB} ()

7. The efficiency of a class A amplifier is

- (a) 25% ()
- (b) 35% ()
- (c) 40% ()
- (d) 60% ()

8. In an amplifier, the negative feedback results in

(a) increase in voltage gain ()

(b) decrease in voltage gain ()

(c) increase in current gain ()

(d) decrease in bandwidth ()

9. _____ oscillator uses a capacitive voltage divider to provide feedback.

(a) Colpitts ()

(b) Hartley ()

(c) Phase-shift ()

(d) Cross-coupled ()

10. The output from CRO is displayed in

(a) 4-dimensional ()

(b) 3-dimensional ()

(c) 2-dimensional ()

(d) 1-dimensional ()

(SECTION : B—SHORT ANSWERS)

(Marks : 15)

Answer *five* questions, taking at least *one* from each Unit :

3×5=15

UNIT—I

1. Explain the significance of forbidden energy gap in brief.
2. Discuss the formation of *n*-type semiconductor.

UNIT—II

3. Explain the operating point of a transistor with a neat diagram.
4. Prove the relation, $\alpha = \frac{\beta}{1 + \beta}$, where the symbols have their usual meanings.

UNIT—III

5. Mention the components and key features of class *B* amplifier.
6. Write the advantages of negative feedback of an amplifier.

UNIT—IV

7. Mention the Barkhausen's criterion required for self-sustained oscillations.
8. Explain the construction of CRT in CRO.

(SECTION : C—DESCRIPTIVE)

(Marks : 50)

Answer five questions, taking at least one from each Unit :

10×5=50

UNIT—I

1. (a) Explain the formation of depletion layer and barrier voltage in *p-n* junction diode. 6
(b) With a neat diagram, illustrate the working of full-wave rectifier. 4
2. (a) Explain in detail the construction, working and application of Zener diode. 6
(b) Describe the principle of filtering action of *L*-filter and *C*-filter. 4

UNIT—II

3. (a) Illustrate with proper diagram, the construction and working of an *N-P-N* transistor. 4
(b) What are the three types of configurations in a transistor? Explain the effect of different V_{CE} values in input characteristics of CE configuration of an *N-P-N* transistor. 6
4. (a) Explain active region, saturation region and cut-off region in output characteristics of CB configuration of a *P-N-P* transistor. 6
(b) Write a note on voltage and power gains of a transistor. 4

UNIT—III

5. (a) What is a multistage transistor amplifier? Draw the circuit diagram of two-stage *R-C* coupled amplifier and explain its operation. 6
(b) With neat diagram, describe the working principle of class *B* push-pull amplifier. 4

6. (a) What is distortion? Mention the causes and reduction of distortion in an amplifier. 6
- (b) How does negative feedback affect the gain and stability of an amplifier? 4

UNIT—IV

7. (a) Explain the construction and operation of phase-shift oscillator. 5
- (b) Write the applications of CRO. Explain the measurement of frequency using CRO. 5
8. (a) Describe electron gun and explain electrostatic focusing in CRO. 5
- (b) Illustrate in detail Hartley oscillator using appropriate circuit diagram. 5